DATE: 25 March DAY: Wednesday .

Bilal Abid Abbasi

ID:- 45961


Hometask

XNOR Gate

Boolean Equation

$$Y = (A \cdot B) + (A' \cdot B') \text{ OR}$$

$$Y = A \cdot B = \overline{A \cdot B}$$

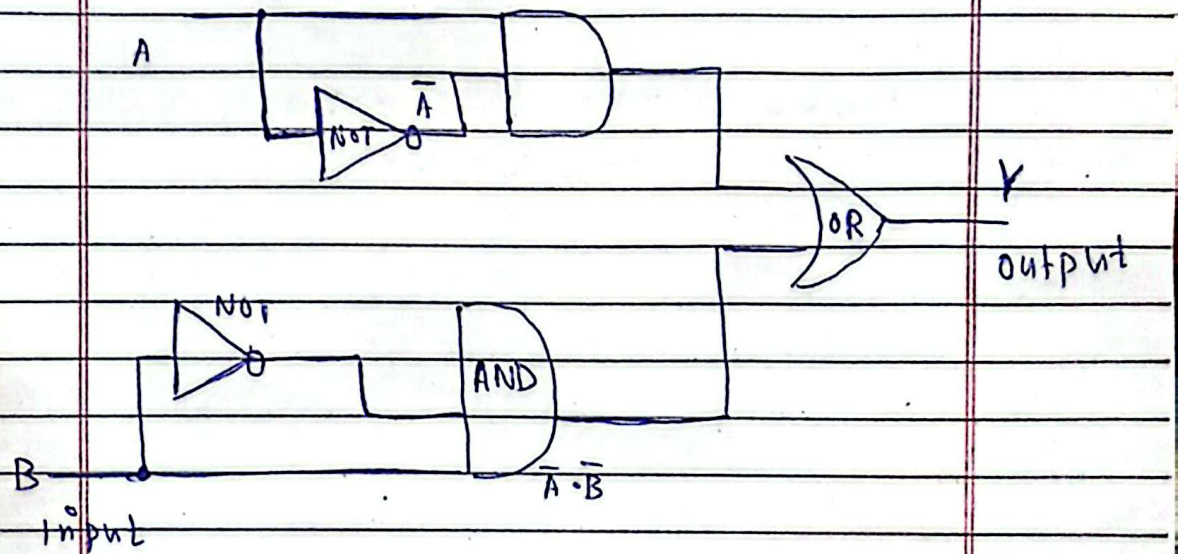

DATE: 25 March DAY: Wednesday

Truth table:

A	B	A ⊕ B (XOR)	Y = XNOR
0	0	0	1
0	1	1	0
1	0	1	0
1	1	0	1

Output is 1 when A = B.

Name:- BILAL Abid Abbasi

ID:- 45961.